

1. Create an equation describing the curved graph that you made on page 90. (Use the method on page 16R.) Remember to make the units balance. Also remember to give evidence in showing that your equation is correct, as explained on pages 16R and 18.
2. According to RS II, if A is proportional to B^C then a one-percent increase in the value of B will cause a ___-percent increase in the value of A. For example, to increase a light bulb current by one percent we must increase the bulb's voltage __%. (Use #1.)
3. We can use that trick to find the slope of a tangent line on the graph of such a relation. Let (B_1, A_1) be the coordinates of a point on the graph where we want to make a tangent line. If we can calculate the coordinates of another point on the graph which is very close to the first one then we can easily find the slope of a line connecting them. If the two points are close together then the curved segment between them will be almost linear and will have nearly the same slope as the tangent line:
 - a. Let B_2 be just 1% greater than B_1 , so that $B_2 = (\text{_____})B_1$. (Insert a number.)
 - b. If the exponent is "3", then A_2 must then be ___ percent greater than A_1 , so that $A_2 = (\text{_____})A_1$.
 - c. In that example the slope of the tangent line must be ___ times A/B .
4. Suppose a certain voltage vs current graph is shaped like a square-root curve, so that V is proportional to I to the ___ power. When the voltage across the device is 6.0 V, the current through it is 0.065 A.
 - a. Using the given data calculate the static resistance of that device.
 - b. Using the trick in #3, show how the dynamic resistance of this device is calculated.
 - c. If we cut the voltage in *half*, the new current will then be _____ times the original current, or _____. The new static resistance will be _____, and the new dynamic resistance will be _____.
Show how those numerical values are calculated, with units.
5. In example 4b the dynamic resistance was equal to the static resistance multiplied by __. In 4c the *new* dynamic resistance is ___ times the *new* static resistance, because the exponent in the relation was ___.
6. In #1 on this page we found that a light bulb's voltage is approximately proportional to the ___ power of its current. Therefore the dynamic resistance of a light bulb must be approximately ___ times its static resistance. Does this result agree with #8 on page 90? ___ Is the ratio of dynamic resistance to static resistance the same for all other points on the graph? ___
7. In Ch. IX we found that the rate at which a device consumes electrical energy is equal to the _____ of its voltage and its current. On page 90 you discovered that a resistor voltage is equal to the product of its _____ and the _____ through it. Write those two equations. (Use "R" to represent the resistance, and "V" and "I" to represent voltage and current.)
 - a. Use the second equation to eliminate the voltage from the first equation, showing how a resistor's heating power can be calculated from its current and resistance. *Check units.* $P = \text{_____}$
 - b. Increasing the resistor current by X% must cause the resistor's heating rate to increase by ____%. (Use #2, above.)
 - c. Show how a resistor's heating rate can be calculated from its *voltage* and resistance.
Begin with the same two equations, and remember to check units.
 - d. Increasing the resistor voltage by Y% causes its *heating rate* to increase by ____% Does #2 agree?
 - e. The two new power formulas (7a and 7c) have been saved in #___ on RS X.
8. In #1 you found that a light bulb voltage is approximately equal to some constant times the _____ of its current. Write that equation, using "k" to represent the constant: $V_b = \text{_____}$
 - a. Use the light bulb equation to eliminate the "V" from the original power formula in #7, showing how the light bulb power can be calculated from "k" and "I": $P = \text{_____}$
 - b. Increasing the current by 0.5% causes a bulb's energy consumption rate to increase by ____%.
9. Suppose I want to use one of the new power formulas to calculate a light bulb's power: Should I use its static resistance, or its dynamic resistance? *Explain your answer.*

1. Almost any two different conducting materials placed in an electrolyte form a "cell". Chemical reactions tend to remove electrons from one material and force them into the other until a certain potential difference is reached. The reaction cannot continue until the potential difference is reduced. The part of a circuit that is outside of the cell is called the "load". You can change the current in a cell by switching to a load with different _____. (measurable *property* that most loads have.)
2. In the experiments on page 84 (reviewed and checked in #3 on page 86) and again in #8 on page 88 we found that that ___creasing the load resistance *greatly* causes the power supply current to ___crease, and the power supply voltage to ___crease slightly. * Give voltages, currents, and load resistances from one of those experiments as evidence. Show how the resistances are calculated.
3. Use a voltmeter, an ammeter, and a big adjustable resistor to make a *voltage vs. current* data table and graph describing the lab power supply. Remember to get your plans approved before you begin, and to make your graph *while* the experiment is in progress. Also remember to cover a *wide* range of currents. A large team works best. Take turns making measurements. *Do not contradict #2.* ___
4. A battery's "terminal voltage" is the potential difference *between its terminals*. A battery is "ideal" if its terminal voltage does *not* depend noticeably on current. *Both* definitions are on RS _____.
 - a. Sketch a voltage vs. current graph describing the behavior of an *ideal* battery.
 - b. How does it differ from the graph you made in #3? *-It has a different* _____.
 - c. Where have we previously seen a voltage vs current graph similar to the one you made in #3? ____
 - d. Does the power supply behave like an ideal battery? _____
 - e. Does it behave like an ideal battery with some other familiar device connected internally? _____
5. Guess what is meant by the "internal resistance" of a cell or battery. (Clue: Its numerical value is *positive*.) If you care to, you can find out from a book if your guess was correct.
- * 6. Explain how a battery's internal resistance can be determined from a graph of terminal voltage vs. current. (This "operational" definition of internal resistance is being saved on RS __.) Illustrate your explanation by using the *graph* from #3 (*NOT* the data table) to determine the internal resistance of the lab power supply in *range* form. Show clearly how the SLV & GLV are calculated in SI units.
- * 7. Construct an equation to describe that same graph, using letters, not numbers. Then give the values of the constants in range form. Then use your equation to estimate (as a range) the maximum current that can be obtained from our lab power supply. *Round off properly*. In explaining your estimate, be sure to mention what load resistance would be required to obtain this current. Also mention the special name given to that kind of load. (Copy it from RS X.) *Try not to contradict your graph*.
8. In 4e we saw that a real battery behaves like an ideal battery with an internal _____ connected in _____. The voltage of the ideal part is called the cell's "electromotive force", or "emf".
 - * a. How can the emf of a cell be determined from its voltage vs. current graph? *Please illustrate*.
 - b. That procedure is an "operational definition" of emf. A copy has been saved on RS _____.
9. How must the terminal voltage of a cell or battery be related to its load voltage? _____ (If this is not obvious then you need to review the definition of "voltage" on page 83R.)
 - * a. Sketch a graph of terminal voltage vs load resistance. (Use 6-8 on p. 92.) Show how you use such a graph to estimate a cell's emf. Then explain why emf is sometimes called "open-circuit voltage".
 - b. Does a cell's emf depend on its load, as terminal voltage does? _____ -Is it a "property" of the cell? _____
10. Four one-ohm resistors are connected in series with four "ideal" one-volt cells:
 - a. Predict the current. (Use page 83R) $I =$ _____
 - b. What is the greatest voltage in this circuit,? _____
 - c. Between which two points is it found? (Label them "A" and "B".)
11. Now the circuit is rearranged as in the second diagram:
 - a. Is the current affected by this alteration? _____
 - b. What is the greatest voltage in the circuit now? _____
 - c. Between what two points is it found? _____
 - d. Suppose there is a switch in the circuit: How much voltage is there between its terminals when the switch is open? _____

