

Date: _____
Page: _____


* QUESTIONS *

1. Define
 - a) Binary Logic
 - b) Logic gate
 - c) Logic function.
2. Explain with symbol, Truth table the basic gates i.e NOT, AND & OR gates.
3. Explain with symbol, Truth table NAND & NOR gates
4. Explain with symbol, Truth table EX-OR & EX-NOR gates.
5. Write a short note on Universal gates.
6. Realise (construct) all the basic gates using only NAND gates.
7. Realise (construct) all the basic gates using only NOR gates.
8. Realise EX-OR & EX-NOR gates using NAND gates
NOR gates

* FILL IN THE BLANKS *

1. Binary logic uses two logic levels i.e logic 0 & logic 1.
2. In + logic HIGH level represents logical 1
3. In - logic LOW level represents logical 0
4. In + logic HIGH level represents logical 0
5. In - logic LOW level represents logical 1.
6. The basic building blocks of Digital circuits are called as logic gates.

Logic function

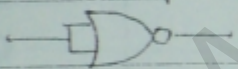- 1. --- explains the input & output relation of logic gates
- 2. The output of NOT gate is always opposite
- 3. If A & B are two inputs, then the output equation of AND gate is $y = A \cdot B$
- 4. If P & Q are two inputs, then the output equation of OR gate is $y = P + Q$
- 5. When we combine AND gate & NOT gate, the resulting gate is NAND
- 6. When we combine OR gate & NOT gate, the resulting gate is NOR
- 7. NAND gate & NOR gates are universal gates
- 8. In Ex-OR gate if all the 'n' input contains odd number of HIGH inputs, then the output will be high
- 9.  is a symbol for NOT gate

* VIVA QUESTIONS *

- 1) What do you mean by logic gates.
- 2) What do you mean by logic function
- 3) Explain the Truth Table of NOT, AND, OR gates.
- 4) Draw the Symbol to represent NOT, AND, OR gates
- 5) What do you mean by NAND gate, explain its Truth Table.
- 6) What do you mean by NOR gate, explain its Truth Table.
- 7) What do you mean by Ex-OR gate, explain its Truth Table.
- 8) What do you mean by Ex-NOR gate, explain its Truth Table.
- 9) What do you mean by Universal gates, give example.
- 10) Realise Ex-OR gate using NAND gates & write T.T. of both gates.
- 11) Realise Ex-NOR gate using NAND gates & write T.T. of both gates.
- 12) Realise ExOR gate using NOR gates & write T.T. of both gates.
- 13) Realise Ex-NOR gate using NOR gates & write T.T. of both gates.
- 14) Identify which gate is this 